

# Basic Verilog RTL

# Module

```
1  module CK1_2 (  
2      clk,  
3      rst_n,  
4      in_1,  
5      in_2,  
6      result  
7  );  
8  
9      input      clk ;  
10     input      rst_n ;  
11     input [7:0] in_1 ;  
12     input [7:0] in_2 ;  
13     output reg [15:0] result;  
14  
15     always @(posedge clk , negedge rst_n) begin  
16         if (!rst_n)  
17             result <= 'd0;  
18         else  
19             result <= in_1 * in_2;  
20     end  
21  
22 endmodule
```

Module frame

Variable declare

Module body

# Basic Syntax

```
1  module CK1_2 (  
2      clk,  
3      rst_n,  
4      in_1,  
5      in_2,  
6      result  
7  );  
8  
9  input      clk ;  
10 input     rst_n ;  
11 input [7:0] in_1 ;  
12 input [7:0] in_2 ;  
13 output reg [15:0] result; //comment style 1  
14  
15 /*  
16  comment style 2  
17  */  
18  
19 always @(posedge clk , negedge rst_n) begin  
20     if (!rst_n)  
21         result <= 'd0;  
22     else  
23         result <= in_1 * in_2;  
24 end  
25  
26 endmodule
```

- End statements with ;

# Basic Syntax

```
1  module CK1_2 (  
2      clk,  
3      rst_n,  
4      in_1,  
5      in_2,  
6      result  
7  );  
8  
9  input      clk ;  
10 input      rst_n ;  
11 input [7:0] in_1 ;  
12 input [7:0] in_2 ;  
13 output reg [15:0] result; //comment style 1  
14  
15 /*  
16  comment style 2  
17 */  
18  
19 always @(posedge clk , negedge rst_n) begin  
20     if (!rst_n)  
21         result <= 'd0;  
22     else  
23         result <= in_1 * in_2;  
24 end  
25  
26 endmodule
```

- Two style of comments
  - Single line comment after “//”.
  - Block comment from “/\*” to “\*/”.

# Basic Syntax

```
1  module CK1_2 (  
2      clk,  
3      rst_n,  
4      in_1,  
5      in_2,  
6      result  
7  );  
8  
9  input      clk ;  
10 input      rst_n ;  
11 input [7:0] in_1 ;  
12 input [7:0] in_2 ;  
13 output reg [15:0] result; //comment style 1  
14  
15 /*  
16  comment style 2  
17 */  
18  
19 always @(posedge clk , negedge rst_n) begin  
20     if (!rst_n)  
21         result <= 'd0;  
22     else  
23         result <= in_1 * in_2;  
24 end  
25  
26 endmodule
```

- Use **begin** ... **end** to compound statements.
- {} is used to combine signals in verilog.

# Declare variable

```
reg      bit;
reg [15:0] data;           // 1 data with bit-width 16
reg [15:0] array [15:0];   // 16 data array with elements' bit-width 16
reg [15:0] matrix [15:0][15:0]; //16*16 data 2d array with elements' bit-width 16

data[7]      //return 7th bit of data.
data[15:8]    //return 8bit signal from data[15] to data[8].
array[3]      //return 3rd element of array.
array[3][5]   //return 5th bit of 3rd element of array.
matrix[7][7]  //return matrix with index [7][7].
```

- <type> [MSB:LSB] <variable>

Type : reg or wire for RTL.

[MSB:LSB]: determine bit width.

# Data type

```
1  module CK1_3 (  
2      clk,  
3      rst_n,  
4      in_1,  
5      in_2,  
6      result  
7  );  
8  
9  input      clk;  
10 input      rst_n;  
11 input [7:0] in_1;  
12 input [7:0] in_2;  
13 output reg [15:0] result;  
14  
15 wire [15:0] mul_tmp;  
16  
17 assign mul_tmp = in_1 * in_2;  
18  
19 always @(posedge clk , negedge rst_n) begin  
20     if (!rst_n)  
21         result <= 'd0;  
22     else  
23         result <= mul_tmp;  
24 end  
25  
26 endmodule
```

- **wire**

- Continuously driven signal.
- Use “**assign**” to assign a value or operations.
- Only for combinational signals.
- **assign** only be used outside always blocks.
- Default type of output ports is **wire**.

# Data type

```
1  module CK1_3 (  
2      clk,  
3      rst_n,  
4      in_1,  
5      in_2,  
6      result  
7  );  
8  
9  input      clk;  
10 input      rst_n;  
11 input [7:0] in_1;  
12 input [7:0] in_2;  
13 output reg [15:0] result;  
14  
15 wire [15:0] mul_tmp;  
16  
17 assign mul_tmp = in_1 * in_2;  
18  
19 always @(posedge clk , negedge rst_n) begin  
20     if (!rst_n)  
21         result <= 'd0;  
22     else  
23         result <= mul_tmp;  
24 end  
25  
26 endmodule
```

- **reg**

- Default is X (unknown).
- Assigned in **always** block.
- For combinational or sequential signals.
- Can not be assigned by 2 or more **always** blocks for RTL design.

Data type	wire	reg
assignment	assign	Always block
Combinational	0	0
Sequential	X	0



# Always Block

```
always @(posedge clk , negedge rst_n) begin
    if (!rst_n)
        result <= 'd0;
    else
        result <= mul_tmp;
end
```

```
reg [15:0] result;

always @(in_1, in_2) begin
    result <= in_1 * in_2;
end
```

- Event driven block.
  - Start procedure if event triggered.
- Can be used for combinational or sequential blocks.

# Blocking and non-blocking assignment

## Blocking assignment (=)

- Execute statements line by line.

```
reg [7:0] A, B;  
  
always @(posedge clk) begin  
    A = B;  
    B = A;  
end
```

- As  $B = A = B$ , A and B will stuck at same value.

## Non-blocking assignment (<=)

- Execute statements at same time.

```
reg [7:0] A, B;  
  
always @(posedge clk) begin  
    A <= B;  
    B <= A;  
end
```

- Swap A and B every cycle.

Highly recommended for sequential circuits.

# Value Representation


```
wire      [15:0] a, b, c;
wire signed [15:0] d;

assign a = 16'b0000000000000000; // assign 16bit 0000000000000000 in binary to a
assign b = 16'h1234;             // assign 16bit          1234 in heximal to b
assign c = 'b0;                  // 'b0 will automatically extend 16'b0 (bit width of c)
assign d = -'d15;                // assign -15 (2's complement) in decimal to d
```

- Value format:  
Constant: <size>'<base><value>  
<size> : bit width.  
<base> : b, o, d, h.  
<value> : value in <base> representation
 
# Bus Concatenation

```
wire [7:0] A;  
wire [7:0] B;  
wire [15:0] C;  
  
assign C = {A[5:0], 2'b00, B};
```



# Operations

```
assign C = A + B; // add
assign C = A - B; // sub
assign C = A * B; // mul
assign C = A / B; // div
assign C = A % B; // mod
assign C = A > B; // greater than
assign C = A < B; // less than
assign C = A & B; // bit-wise and
assign C = A | B; // bit-wise or
assign C = A ^ B; // bit-wise XOR
assign C = A && B; // logical and
assign C = A || B; // logical or
assign C = A << B; // shift left
assign C = A >> B; // shift right
```

# Signed Issue


```
wire [7:0] A;  
wire [3:0] B;  
wire [7:0] C;  
  
assign C = A + B;
```

- B will be zero extended to 8 bits.

```
wire signed [7:0] A;  
wire signed [3:0] B;  
wire signed [7:0] C;  
  
assign C = A + B;
```

- B will be sign extended to 8 bits.
- Both operands must be signed.


# Combinational Circuit

 

```
1  module CK2_1 (  
2      in_1,  
3      in_2,  
4      in_3,  
5      out_1,  
6      out_2  
7  );  
8  
9  input  in_1, in_2, in_3;  
10 output out_1, out_2;  
11  
12 assign out_1 = in_1 | in_2;  
13 assign out_2 = in_2 & in_3;  
14  
15 endmodule
```

```
1  module CK2_1 (  
2      in_1,  
3      in_2,  
4      in_3,  
5      out_1,  
6      out_2  
7  );  
8  
9  input      in_1, in_2, in_3;  
10 output reg out_1, out_2;  
11  
12 always @(in_1, in_2, in_3) begin  
13     out_1 = in_1 | in_2;  
14     out_2 = in_2 & in_3;  
15 end  
16  
17 endmodule
```

# Combinational Circuit

 

```
1  module CK2_1 (  
2      in_1,  
3      in_2,  
4      in_3,  
5      out_1,  
6      out_2  
7  );  
8  
9  input      in_1, in_2, in_3;  
10 output reg out_1, out_2;  
11  
12 always @(in_1, in_2, in_3) begin  
13     out_1 = in_1 | in_2;  
14     out_2 = in_2 & in_3;  
15 end  
16  
17 endmodule
```




recommended

```
1  module CK2_1 (  
2      in_1,  
3      in_2,  
4      in_3,  
5      out_1,  
6      out_2  
7  );  
8  
9  input      in_1, in_2, in_3;  
10 output reg out_1, out_2;  
11  
12 always @(*) begin  
13     out_1 = in_1 | in_2;  
14     out_2 = in_2 & in_3;  
15 end  
16  
17 endmodule
```



# If-else

 

```
module CK2_2 (  
    in_1,  
    in_2,  
    sel,  
    out,  
);  
  
input    in_1, in_2, sel;  
output reg out;  
  
always @(*) begin  
    if (sel == 'b0)  
        out = in_1;  
    else  
        out = in_2;  
end  
  
endmodule
```

```
1 module CK2_3 (  
2     in_1,  
3     in_2,  
4     sel,  
5     out,  
6 );  
7  
8 input    in_1, in_2, sel;  
9 output    out;  
10  
11 assign out = (sel == 'b0)? in_1 : in_2;  
12  
13 endmodule
```

in-line style


# Case

```
1  module CK2_4 (  
2      in_1,  
3      in_2,  
4      in_3,  
5      in_4,  
6      sel,  
7      out,  
8  );  
9  
10 input      in_1, in_2, in_3, in_4;  
11 input [2:0] sel;  
12 output reg out;  
13  
14 always @(*) begin  
15     case (sel)  
16         'd0 : out = in_1;  
17         'd1 : out = in_2;  
18         'd2 : out = in_3;  
19         'd3 : out = in_4;  
20         default: out = 'b0;  
21     endcase  
22 end  
23  
24 endmodule
```


# ALU with Case

```
1  module CK2_5 (  
2      src1,  
3      src2,  
4      op,  
5      result,  
6  );  
7  
8  input    [7:0]  src1, src2;  
9  input    [2:0]  op;  
10 output reg [7:0] result;  
11  
12 always @(*) begin  
13     case (op)  
14         'd0    : result = src1 + src2;  
15         'd1    : result = src1 - src2;  
16         'd2    : result = src1 & src2;  
17         'd3    : result = src1 | src2;  
18         default : result = 'b0;  
19     endcase  
20 end  
21  
22 endmodule
```

# Sequential circuit

 
 
```
reg Q;  
  
always @(posedge clk) begin  
    if (reset)  
        Q <= 'b0;  
    else  
        Q <= D;  
end
```




- Active high and Synchronous reset

# Synchronous and Asynchronous Reset

 
## Synchronous & active high

```
reg Q;  
  
always @(posedge clk) begin  
    if (reset)  
        Q <= 'b0;  
    else  
        Q <= D;  
end
```





 
## Asynchronous & active high


```
reg Q;  
  
always @(posedge clk, posedge reset) begin  
    if (reset)  
        Q <= 'b0;  
    else  
        Q <= D;  
end
```



# Finite State Machine (FSM)

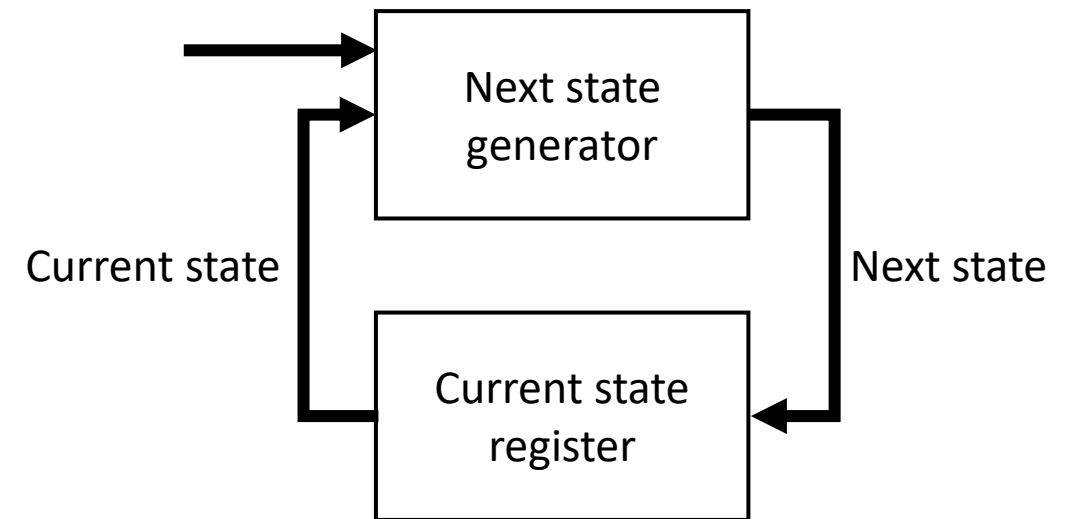  

# Finite State Machine (FSM)

 

```
localparam S_IDLE   = 'd0;
localparam S_IN     = 'd1;
localparam S_EXE    = 'd2;
localparam S_OUT    = 'd3;

reg [1:0] current_state, next_state;
```



```
always @(posedge clk, negedge rst_n) begin
    if (!rst_n)
        current_state <= S_IDLE;
    else
        current_state <= next_state;
end
```

sequential

```
always @(*) begin
    case (current_state)
        S_IDLE : if (in_valid) next_state = S_IN;
                  else         next_state = S_IDLE;
        S_IN   : if (in_valid) next_state = S_IN;
                  else         next_state = S_EXE;
        S_EXE  : if (done)     next_state = S_OUT;
                  else         next_state = S_EXE;
        S_OUT  :              next_state = S_IDLE;
        default : next_state = S_IDLE;
    endcase
end
```

combinational

# Finite State Machine (FSM)

  

```
localparam S_IDLE = 'd0;
localparam S_IN   = 'd1;
localparam S_EXE  = 'd2;
localparam S_OUT  = 'd3;
```

```
reg [1:0] current_state, next_state;
```

```
always @(posedge clk, negedge rst_n) begin
    if (!rst_n)
        current_state <= S_IDLE;
    else
        current_state <= next_state;
end
```

```
always @(*) begin
    case (current_state)
        S_IDLE : if (in_valid) next_state = S_IN;
                  else        next_state = S_IDLE;
        S_IN   : if (in_valid) next_state = S_IN;
                  else        next_state = S_EXE;
        S_EXE  : if (done)     next_state = S_OUT;
                  else        next_state = S_EXE;
        S_OUT  :              next_state = S_IDLE;
        default : next_state = S_IDLE;
    endcase
end
```

combinational




# for loop example

```
integer i;
reg [31:0] tmp[31:0];

always @(posedge clk, negedge rst_n ) begin
    if (!rst_n) begin
        for (i = 0; i < 32; i = i + 1) begin
            tmp[i] <= 'd0;
        end
    end else begin
        /*
        something else
        */
    end
end
```

# Testbed

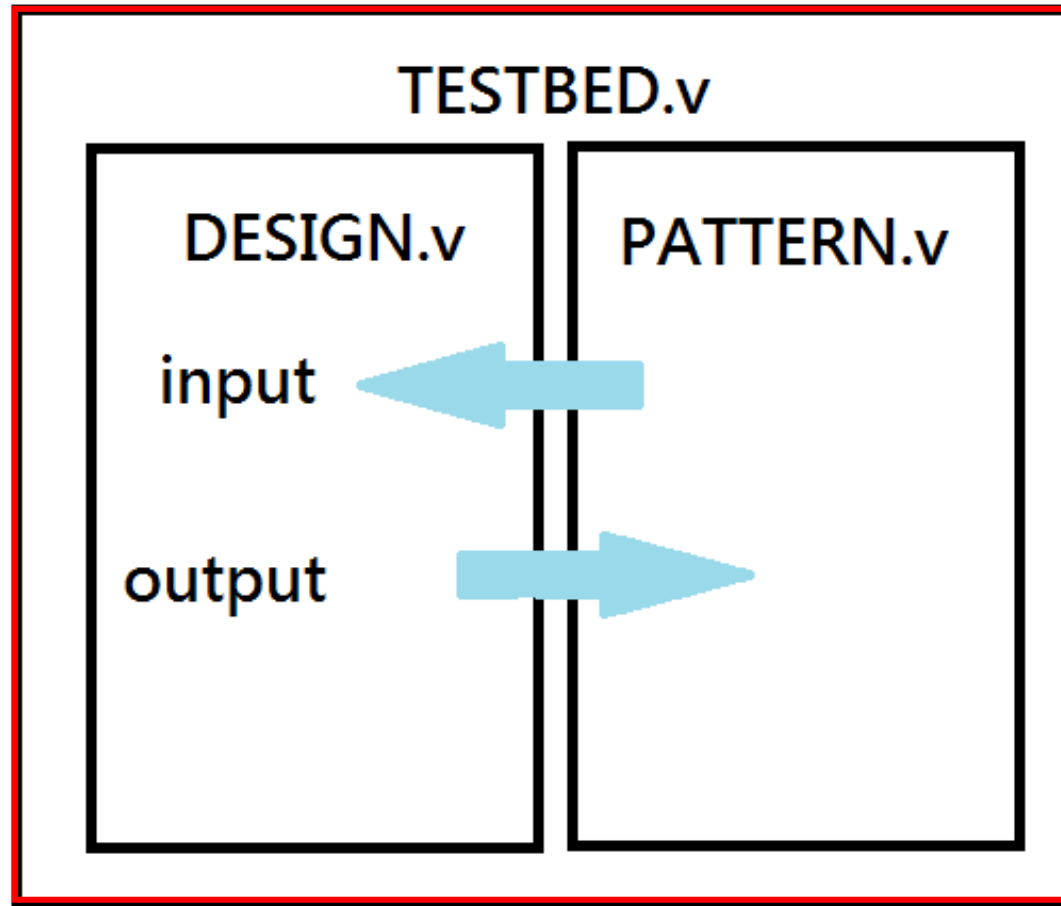

```
module TESTBED;


// wire connection
wire clk,rst_n,in_valid,out_valid,mem_wen;
wire [11:0] mem_addr;
wire [31:0] inst,mem_dout,inst_addr,mem_din;

SP My_SP(
    .clk(clk),
    .rst_n(rst_n),
    .in_valid(in_valid),
    .out_valid(out_valid),
    .mem_wen(mem_wen),
    .inst(inst),
    .mem_dout(mem_dout),
    .inst_addr(inst_addr),
    .mem_addr(mem_addr),
    .mem_din(mem_din)
);


MEM My_MEM(
    .Q(mem_dout),
    .CLK(clk),
    .CEN(1'b0),
    .WEN(mem_wen),
    .A(mem_addr),
    .D(mem_din),
    .OEN(1'b0)
);

PATTERN My_PATTERN(
    .clk(clk),
    .rst_n(rst_n),
    .in_valid(in_valid),
    .out_valid(out_valid),
    .inst(inst)
```

# Testbed

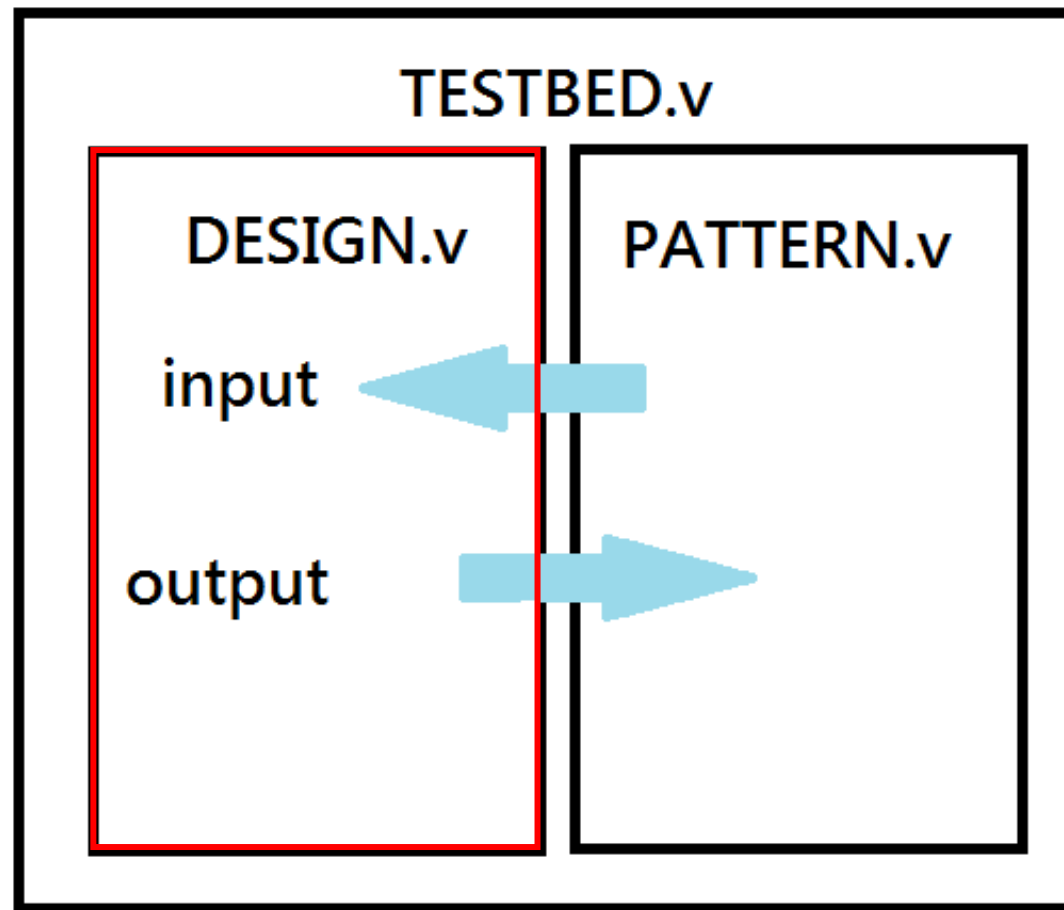

# Testbed

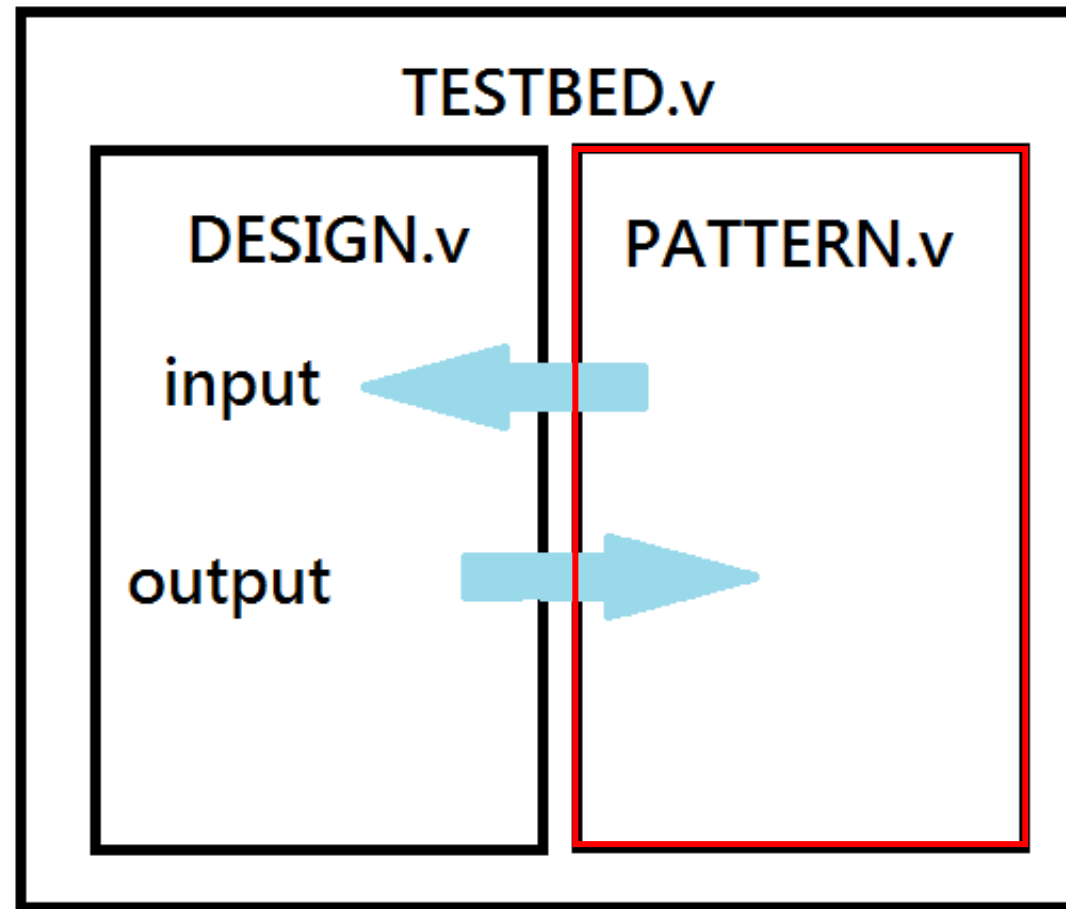

# Recommended Text Editor


- VS code with Verilog extension
- Notepad++
- Sublime

# Testbench and Pattern

# Port declaration

```
module PATTERN(  
    // Output Signals  
    clk,  
    rst_n,  
    in_valid,  
    inst,  
    // Input Signals  
    out_valid,  
    inst_addr  
);  
  
//=====  
//   Input and Output Declaration  
//=====  
  
output reg clk,rst_n,in_valid;  
output reg [31:0] inst;  
  
input wire out_valid;  
input wire [31:0] inst_addr;
```

TESTBED.v

 

```
SP My_SP(  
    .clk(clk),  
    .rst_n(rst_n),  
    .in_valid(in_valid),  
    .out_valid(out_valid),  
    .mem_wen(mem_wen),  
    .inst(inst),  
    .mem_dout(mem_dout),  
    .inst_addr(inst_addr),  
    .mem_addr(mem_addr),  
    .mem_din(mem_din)  
);  
  
MEM My_MEM(  
    .Q(mem_dout),  
    .CLK(clk),  
    .CEN(1'b0),  
    .WEN(mem_wen),  
    .A(mem_addr),  
    .D(mem_din),  
    .OEN(1'b0)  
);  
  
// modify "PATTERN My_PATTERN" to "PATTERN_p My_PATTERN" for pipelined design  
PATTERN My_PATTERN(  
    .clk(clk),  
    .rst_n(rst_n),  
    .in_valid(in_valid),  
    .out_valid(out_valid),  
    .inst(inst),  
    .inst_addr(inst_addr)  
);
```

# Variable declaration

```
//=====
// parameters & integer
//=====

integer pat_num = 1000, out_max_latency = 10, seed = 64;
integer i, t, pat, out_counter;
integer golden_inst_addr;          // ***** Program Counter ***** //
integer instruction [999:0];       // ***** Instruction (from inst.txt) ***** //
integer opcode, rs, rt, rd, shamt, func, immediate, address;
integer golden_r [31:0];           // ***** Gloden answer for Reg ***** //
integer mem [4095:0];              // ***** Data Memory (from mem.txt) ***** //
```

```
// read data mem & instruction
$readmemh("instruction.txt", instruction);
$readmemh("mem.txt", mem);
```



# Initial / task block

```
//=====
// initial
//=====

initial begin
    // read data mem & instrction
    $readmemh("instruction.txt", instruction);
    $readmemh("mem.txt", mem);
    // initialize control signal
    rst_n = 1'b1;
    in_valid = 1'b0;
    // initial variable
    golden_inst_addr = 0;
    for(i = 0; i < 32; i = i + 1)begin
        golden_r[i] = 0;
    end
    // inst=X
    inst = 32'bX;
    // reset check task
    reset_check_task;
    // generate random idle clk
    t = $random(seed) % 3 + 1'b1;
    repeat(t) @(negedge clk);
    // main pattern
    for(pat = 0; pat < pat_num; pat = pat + 1)begin
        input_task;
        out_valid_wait_task;
        check_ans_task;
    end
    check_memory_task;
    display_pass_task;
end
```

```
//=====
// task
//=====

// reset check task
> task reset_check_task; begin...
end endtask

// input task
> task input_task; begin...
end endtask

// out_valid wait task
> task out_valid_wait_task; begin...
end endtask

// check_ans_task
> task check_ans_task; begin...
end endtask

// check_memory_task
> task check_memory_task; begin...
end endtask

// display fail task
> task display_fail_task; begin...
end endtask

// display pass task
> task display_pass_task; begin...
end endtask
```

# Input data / Output data check

```
// input task
task input_task; begin
    // inst = ? ,in_valid = 1
    inst = instruction[golden_inst_addr >> 2];
    in_valid = 1'b1;
    @(negedge clk);

    // inst = x ,in_valid = 0
    inst = 32'bX;
    in_valid = 1'b0;
end endtask
```

Input data change at negedge clk

Register value "r[]"  
From your  
design

Generate answer from your pattern

```
// check register
for(i=0;i<2;i=i+1)begin
    if(My_SP.r[i] != golden_r[i])begin
        display_fail_task;
        $display("-----");
        $display("PATTERN NO.%4d",pat);
        $display("register [%2d] error",i);
        $display("answer should be : %d , your answer is : %d",golden_r[i],My_SP.r[i]);
        $display("-----");
        repeat(2) @(negedge clk);
        $finish;
    end
end
```

Check output data at  
negedge clk

# Function validation

## check\_ans\_task

```
// answer calculate
opcode = instruction[golden_inst_addr_out>>2][31:26];
rs = instruction[golden_inst_addr_out>>2][25:21];
// R-type
// I-type
// PC & jump, beq...etc.
// hint: it's necessary to consider sign extension while calculating
/*

    Complete your function validation here

*/
```

input\_task

```
// PC
opcode = instruction[golden_inst_addr_in>>2][31:26];
rs = instruction[golden_inst_addr_in>>2][25:21];
// You can calculate golden_inst_addr_in is (triggered by Jump, beq...etc.) or (PC + 4), as a check for design output inst_addr
// PC & jump, beq...etc.
// hint: it's necessary to consider sign extension while calculating
/*
    Complete your function validation here
*/
```